

Main components	
STLUX385A	Digital controller for lighting and power supply applications
STEVAL-ILL066V1 (ex. STEVAL385LEDPSR)	100W LED street lighting demonstration board using STLUX385A

Specification

- Two output channels
- Output power, 48W for channel (total 96W)
- Output 2x60V maximum
- Output 2x800mA maximum
- Analog dimming algorithm from 10mA to 800mA, same as the ILL066V1 demo board
- Same lout on the two channels

Circuit description

This document describes in detail the modification of the STEVAL-ILL066V1 demo board to implement two output LEDs channels (or more if the number of output channels is increased).

This Design Note describes how to drive two output channels but the same procedure is usable for a different numbers of output channels. A limitation is given by both the half voltage of half bridge power supply applied to the output transformer and the maximum output power of the PFC stage used on the board. The board is depicted in [Figure 1](#).

The output voltage automatically adapts to the required load; the verified output range is from 20V to 60V. The output current is the same for the two output circuits and, for this application, there is no way to regulate a different output current on the two output channels. NOTE: if an output circuit is short circuited, the other output circuit is not affected by this.

The circuit modification applies only to the output schematics sheet available with the AN4382 as showed in [Figure 2](#). The two channel output circuits are showed in [Figure 3](#). To clarify the page schematics, each main function is highlighted by a red area.

The half bridge driver and MOSFET highlighted in **area 1** is exactly the same for the two output channels showed in [Figure 3](#). Only the shunt resistor is modified to adapt the maximum output current to 800mA. In this case the R36 and R37 resistors are changed to 1.69 Ω . The resonant inductor (T1) is the same as the original circuit.

The **area 2** is the shunt resistor for S_CH0 signal. The S_CH0 signal is acquired by the ADC channel of STLux and the level is function of the output voltage of the output transformer (via pins 6 and 7). The S_CH0 signal is used to protect the output capacitor when the load (LEDs in series) is not connected or is opened. The same function is implemented when two channels are used. In this case and for this circuit, when one of the two loads is open the other channel is powered off. If the user wants to preserve the function for the available single channel, a short circuit (MOSFET with drivers) is applied to the pin 3 and 5 of the output transformers (T2 or T8) with the “no load” condition. In order to detect the open channel, STLux must monitor two S_CH0 circuit (not present in [Figure 3](#)). Another option to detect it is to implement two or more opto coupler reporting the output voltage measure to STLUX. If the user wants to preserve the single output channel when the others are opened, the circuit defined in [Figure 3](#) is not applicable. The **area 3** output is the S_CH0 signal and R102 and R103 resistors in [Figure 3](#) are simple voltage adders. To change the maximum output voltage, a PSR parameters library is available using the “in” or “ip” serial command (parameter #48 - “no load S_CH0”).

The **area 4** is the isolated output circuit and is the same for the two outputs. Please note that the secondary GND connected together for the two outputs in this area can also be divided. In this case the two output channels can be serially connected allowing so to reduce the output pins.

Figure 1. Modified board

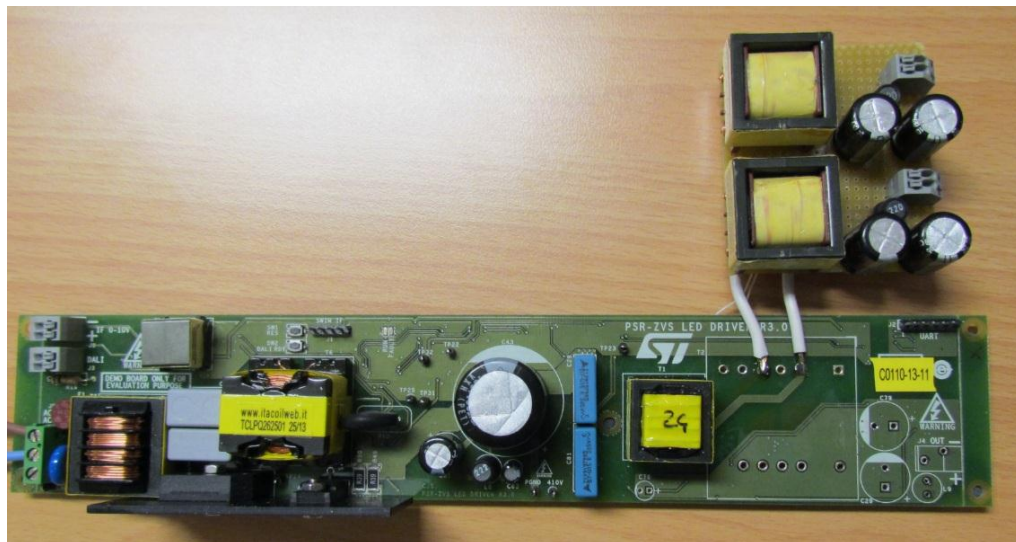


Figure 2. AN4382 - original circuit diagram



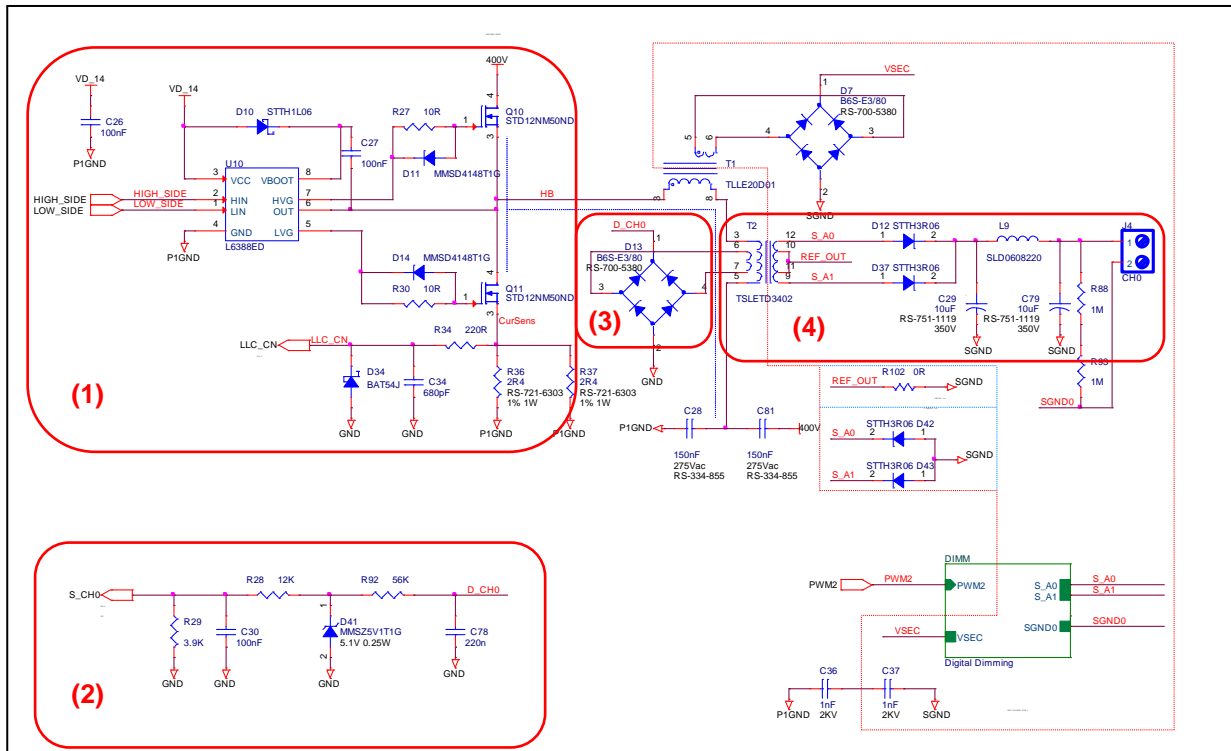


Figure 3. Modify circuit diagram for two channels

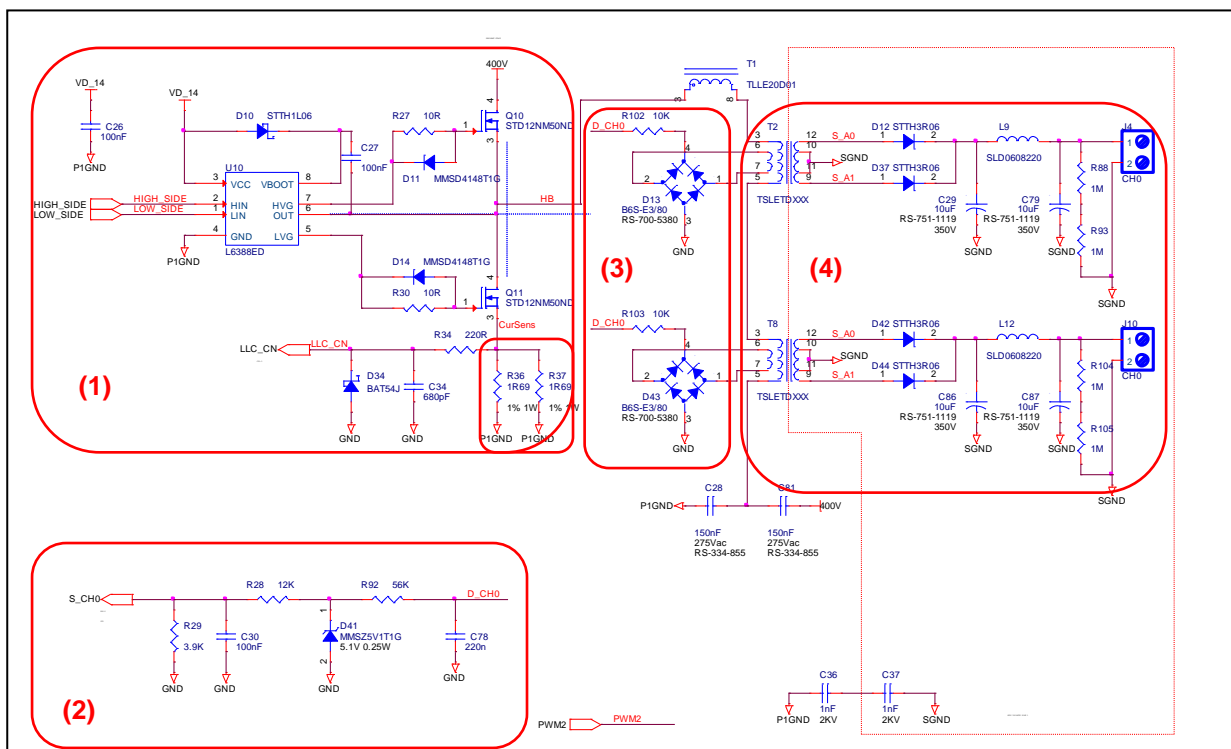

The output transformer used in this design is specified in [Figure 4](#) and the output voltage is, at maximum, equal to 60V. Instead of having a 1A output current as the regular application, when typing “// 3450” at command line for this transformer you get an output current equal to 690mA. Please refer to [Table 1](#) to identify the new output current.

Figure 4. Output transformer - example

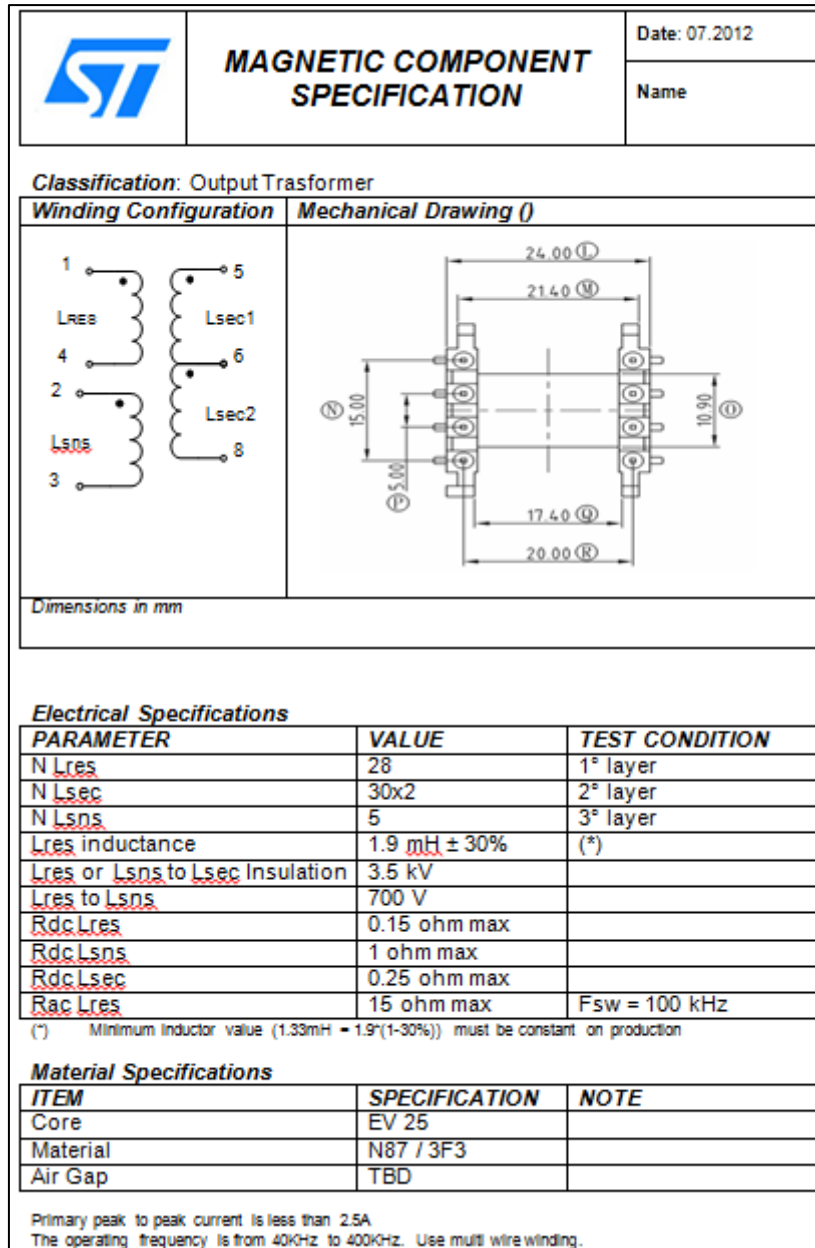

Measurement results

The load of the two output channels is a "CROMA 63101-63105-6312" Used in "CV" mode to fix the output voltage.

The modification proposed in this document allows the board to have an output current and output voltage as defined in [Table 1](#)

Table 1. Output current at different level and total board efficiency

"II" command	Pwin (W)	CH1		CH2		Efficiency
		Iout (mA)	Vout (V)	Iout (mA)	Vout (V)	
660	8.87	60	60	59	60	0.805
795	17.28	122	60	122	60	0.847
935	26.05	187	60	186	60	0.859
1070	33.44	238	60	238	60	0.854
1380	45.6	337	60	337	60	0.887
1770	53.88	405	60	405	60	0.902
2175	62.64	473	60	472	60	0.905
2600	71.8	543	60	543	60	0.908
3020	81.26	615	60	615	60	0.908
3450	90.96	690	60	690	60	0.910
3750	97.87	743	60	743	60	0.911
4070	105.18	800	60	800	60	0.913

When changing the Vout for a single channel, an Iout mismatch can be seen as shown in [Table 2](#).

Table 2. Iout mismatch vs Vout variation

"II" cmd	Pwin	CH1		CH2		Efficiency
		Iout (mA)	Vout (V)	Iout (mA)	Vout (V)	
4070	72.90	810	20	801	60	0.881
4070	80.91	806	30	799	60	0.891
4070	89.99	803	40	799	60	0.890
4070	97.50	800	50	798	60	0.901
4070	105.18	800	60	800	60	0.913

Variations

In order to see the results described above for the ILL066V1 demo board, a firmware update is needed to V3R29. No change is needed to the source code and to the file configuration. For this demo board the DALI and the 0-10V interfaces must be disabled because the output current is related to the original ILL066V1 (1CH only).

The relation of the output current respect to the “I” command is depicted in [Table 1](#). This is the only difference respect to what’s defined in the AN4382.

Support material

Related design support material
STWS-PSRDEMO-V3R29, source code for STEVAL-ILL066V1 or STEVAL385LEDPSR
Documentation
Datasheet: STLUX385A - Digital controller for lighting and power supply applications
Application note: AN4382 - 100 W LED street lighting application using STLUX385A
STEVAL385LEDPSR Library - Application Note

Revision history

Date	Version	Changes
03-Mar-2014	1	Initial release

Please Read Carefully

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at anytime, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

ST PRODUCTS ARE NOT DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2014 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com