

STEVAL-ILL066V1 PCB layout guidance

By Francesco Ferrazza and Ambrogio D'adda

Main components	
STEAVL-ILL066V1	100w PSR-ZVS streetlight demo board
STLUX385A	State Machine Event Driven digital controller

Purpose and benefits

STEVAL-ILL066V1 is a complete and configurable solution for high efficient single string high brightness LED driver. For different application, customers need to modify the eval board. A general layout guidance is provided by this design tip and is used when a new PCB is requested.


For detailed schematic, please refer to AN4461.

Description

The first suggestion is to identify the power signal respect the low energy signal (or high impedance signal). Make this two-signal type separately from one to another using the maximum distance available.


The suggested GND connection is schematized on the [Figure 1](#).


Figure 1. PCB block diagram connection

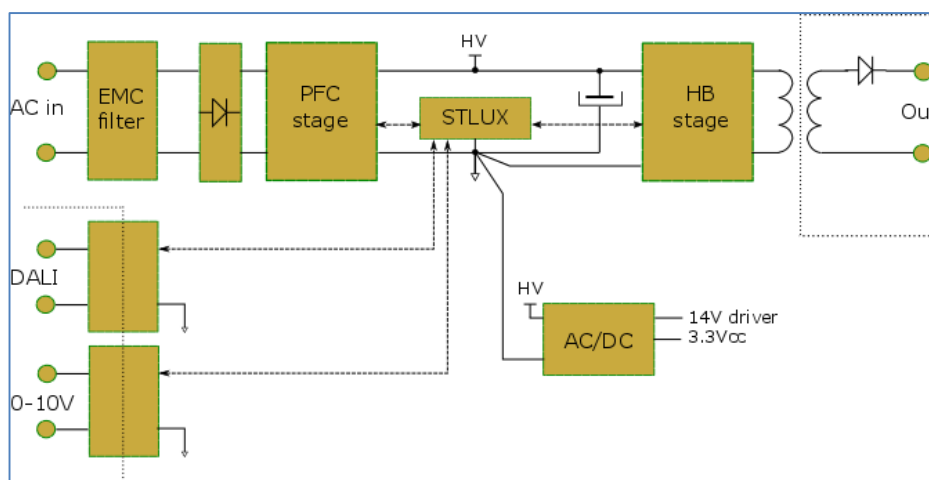

Identify the high voltage current loop (the PFC Drain MOSFET or the Half Bridge middle point on this topology) and create a good isolation around this signal without any interference of the STLUX analog signal. Use a wire track width compatible with the current on the track. The high current loop is identified on [Figure 2](#) and [Figure 3](#). On the same figure is also evidenced the high $\Delta V/\Delta T$ signal (the MOSFET gate pin signal). On these signals, the suggestion is to put the driver near the MOSFET gate to minimize the signal distortion.

Figure 2. PFC current loop

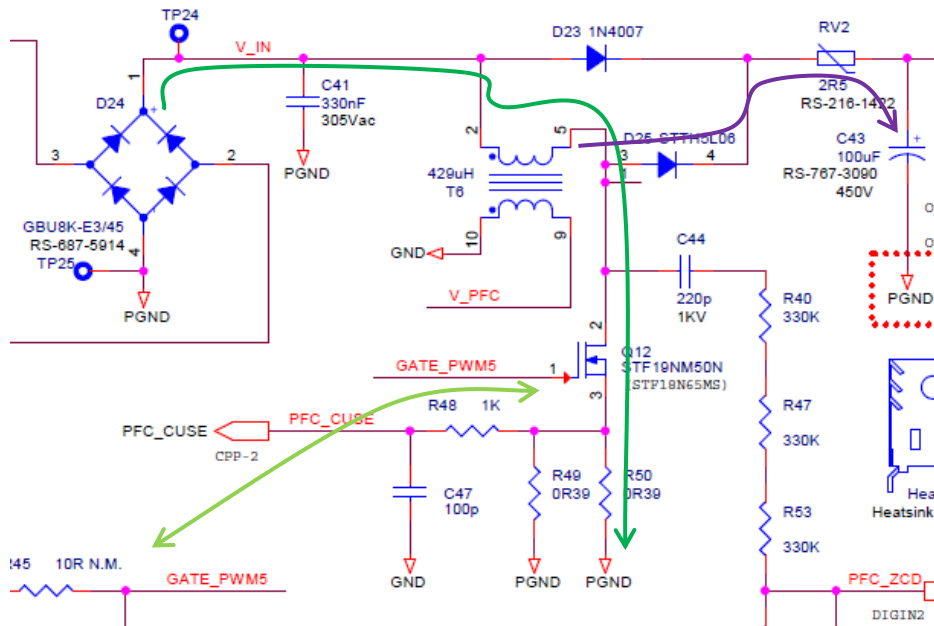

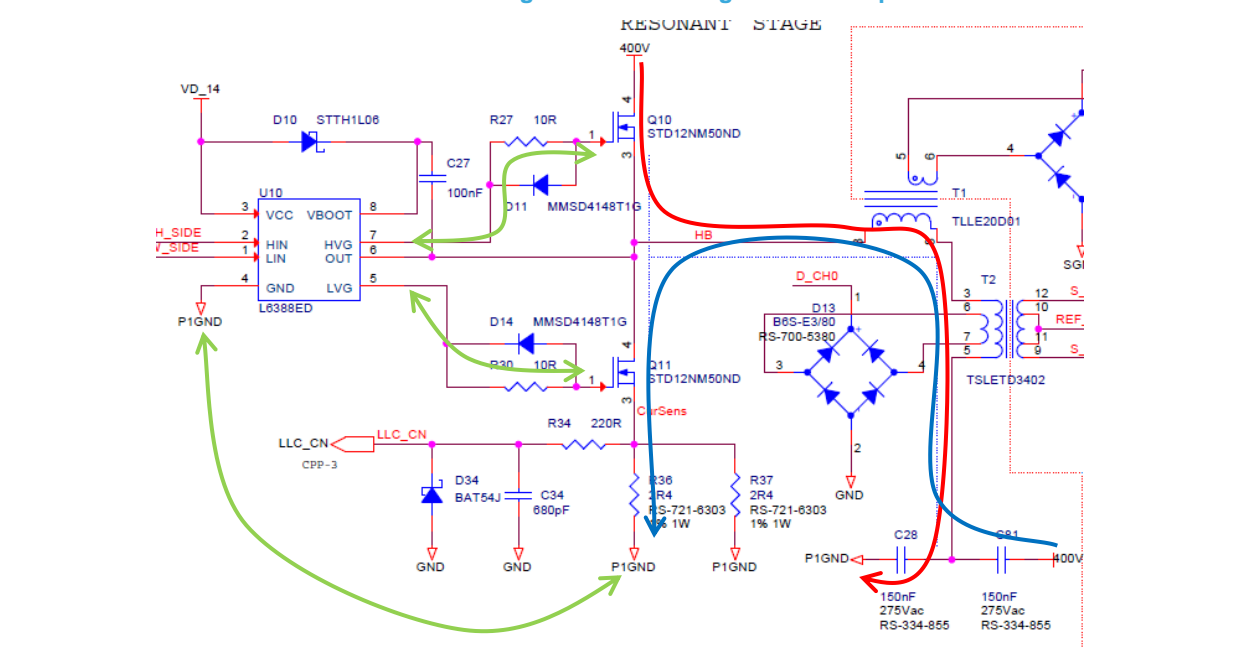

Do not put the high impedance signal under the power inductor.

A particular note for the analog signal acquired by the STLUX (any signal connected to the ADC and Comparators). Protect this wire from the influence of the high current signal. The comparator input signal is a 50nS detection signal, any spike is potentially detected by the STLUX.

The CN_CNT, LLC_CN, PFC_CUSE and PFC_ZCD signal is the more critical signal on the board. Protect and isolate the wiring track on the PCB from all others signal.

Put the U18 (THD optimizer circuit) near the PFC sensing resistor to minimize any ground variation.

Do not use flood on the power area and vice versa, use flood on the STU/IX area

Put the AC/DC converter into a dedicated area and use the maximum distance respect the STLUX area. This minimize the influence of the AC/DC spike on the SLTUX analog signal.

Support material

Related design support material
EVAL board STEAVL-ILL066V1
Documentation
Datasheet STLUX385A
Application note, AN4461

Revision history

Date	Version	Changes
27-Oct-2015	1	Initial release

Please Read Carefully

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at anytime, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

ST PRODUCTS ARE NOT DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2016 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com